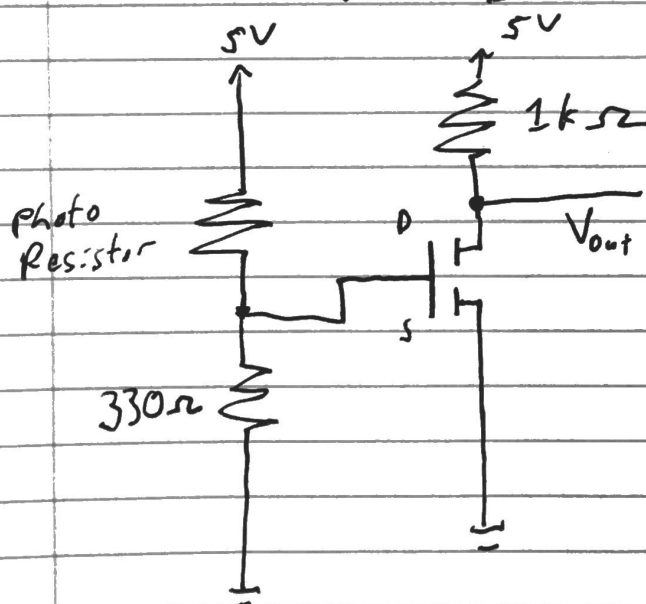


Finger Trigger Circuit

*Note: this resistor determines sensitivity of MOSFET to flexing



On hit, $V_{out} = \text{LOW}$
 On miss, $V_{out} = \text{HIGH (5V)}$

Photo Resistor Receiver Sensor